

Assignment 1 (15 Marks-7.5%)

SEC NO	Date for Showing the output to Instructor	Due Date for final submission through CMS
1	14 th October 11:00 AM only	By 15/10/2020 11:00 PM

Delay on showing the output or submission will lose 20% for every one-day delay from the due date.

Team Details:

Terminal No: 3

Sl No	Name	ID No
1	Kaushik Kalakonda	2020A3PS0468H

Problem Statement: Design a state machine to control the tail lights of a 1965 Ford Thunder bird (Figure 1). The tail lights are composed of three lights on each side which operate for the turns as shown in figure 2. The state machine has two inputs (**LEFT**, **RIGHT**) and 6 outputs (**LC**, **LB**, **LA**, **RA**, **RB** and **RC**). When (**RIGHT=0** and **LEFT=0**) or when (**RIGHT=1** and **LEFT=1**) no lights will turn ON. If (**RIGHT=0** and **LEFT=1**) then lights **LC**, **LB**, and **LA** will be ON as shown in figure 2(a) indicating **LEFT** turn. If (**RIGHT=1** and **LEFT=0**) then lights **RA**, **RB**, and **RC** will be ON as shown in figure 2(b) indicating **RIGHT** turn. In addition to **LEFT** and **RIGHT** there are two more inputs **Clk** and **Reset** for normal operation of FSM. When **Reset** is enabled all lights will be OFF. The flashing rate of LEDs is 2Hz (or 4Hz) (i.e. the time between two successive states is 0.5s (or 0.25s)).

 


Figure 1

Left Turn

Right Turn

 



Figure 2(a)

Figure 2(b)

Figure 2

(Please refer to the file named “Vivado_Design_Flow_All_Steps.pdf” for a review of all the steps in the design flow)

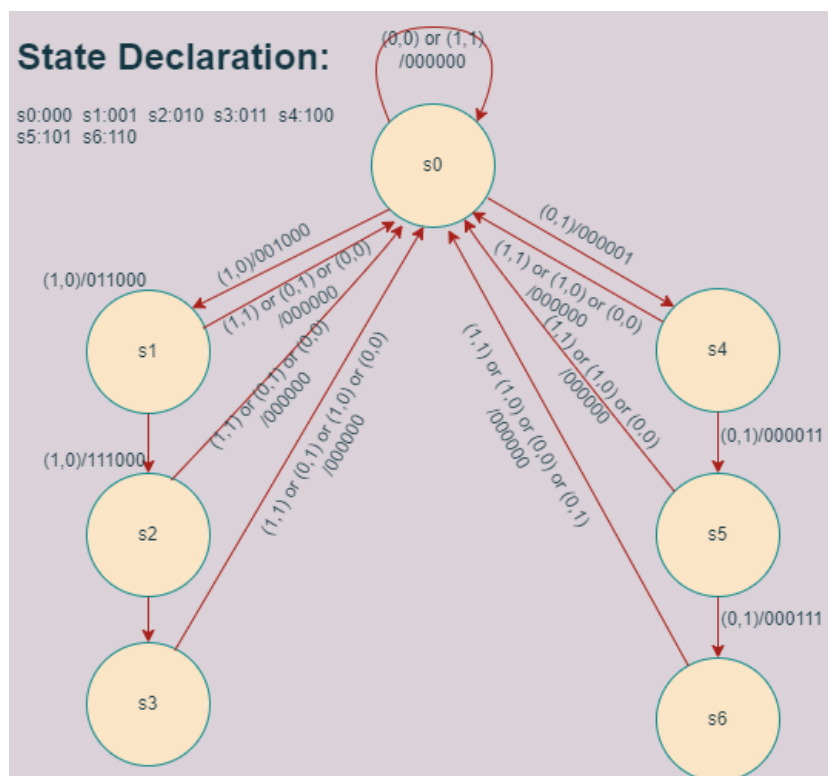1. **Question:** Draw the FSM (can be an image) with proper description.



Answer:

2. Create a Vivado Project and write Verilog code (**Car_FSM.v** with comments) for implementing the above FSM.

Question: Paste the image of verilog code Car_FSM.v.

Answer:

```
1  `timescale 1ns / 1ps
2
3  module Car_FSM(
4
5      input clk,
6      input reset,
7      input left,
8      input right,
9      output reg [2:0] l,
10     output reg [2:0] r
11 );
12
13 //clock divisions for 1 MHz / 2^27 = 2-4 Hz
14 reg [26:0] clk_div;
15 always@(posedge clk, negedge reset)
16 begin
17     if(reset==1)
18         clk_div=0;
19     else
20         clk_div=clk_div+1;
21     end
22
23 //present and next states
24 reg [2:0] ps, ns;
25
26 //states of the fsm
27 parameter s0 = 3'b000,s1 = 3'b001,s2 = 3'b010,s3 = 3'b011,s4 = 3'b100,s5 = 3'b101,s6 = 3'b110;
28
29 always @(posedge clk_div[26], negedge reset)
30 begin
31     if (reset ==1)
32         ps=s0;
33     else
34         ps <= ns;
35     end
36
37 //following the flow model of the fsm
38 always @(ps, left, right)
39 begin
40     case (ps)
41         s0 : begin
```

```

40 case (ps)
41     s0 : begin
42         if (left==0 && right==1)
43             ns = s1;
44         else if (left==1 && right==0)
45             ns = s4;
46         else
47             ns = s0;
48         end
49     s1 : begin
50         if (left==0 && right==1)
51             ns = s2;
52         else
53             ns = s0;
54         end
55     s2 : begin
56         if (left==0 && right==1)
57             ns = s3;
58         else
59             ns = s0;
60         end
61     s3 : begin
62         ns = s0;
63         end
64     s4 : begin
65         if (left==1 && right==0)
66             ns = s5;
67         else
68             ns = s0;
69         end
70     s5 : begin
71         if (left==1 && right==0)
72             ns = s6;
73         else
74             ns = s0;
75         end
76     s6 : begin
77         ns = s0;
78         end
79 endcase
80 end

```

```

81 :
82 //output of the lights at the present state of the fsm
83 always @(ps)
84     case (ps)
85     s0 : begin
86         l = 3'b000;
87         r = 3'b000;
88     end
89     s1 : begin
90         l = 3'b000;
91         r = 3'b001;
92     end
93     s2 : begin
94         l = 3'b000;
95         r = 3'b011;
96     end
97     s3 : begin
98         l = 3'b000;
99         r = 3'b111;
100    end
101    s4 : begin
102        l = 3'b001;
103        r = 3'b000;
104    end
105    s5 : begin
106        l = 3'b011;
107        r = 3'b000;
108    end
109    s6 : begin
110        l = 3'b111;
111        r = 3'b000;
112    end
113    endcase
114 :
115 endmodule
116

```

3. Write the test bench **Test_Car_FSM.v** and simulate your design to check the functionality.

Question: Paste the image of test bench verilog code **Test_Car_FSM.v**.

```

module Test_Car_FSM(
);
  reg left;
  reg right;
  reg Reset;
  reg Clk;
  wire [2:0] l;
  wire [2:0] r;

  Car_FSM al(Clk, Reset, left, right, l, r);

  initial
  begin
    Clk=0;
    repeat(50)
    #5 Clk=~Clk;
    $finish;
  end

  initial
  begin
    Reset=1'b1;#20
    left=1'b1;right=1'b0;
    Reset=1'b0;
    #50 Reset=1'b1;
    #20 Reset=1'b0;
    left=1'b0;right=1'b1;
    #50 Reset=1'b1;
    #20 Reset=1'b0;
    left=1'b1;right=1'b1;
    #50 Reset=1'b1;
    #20 Reset=1'b0;
    left=1'b0;right=1'b0;
  end


endmodule

```

Answer:

Question: Paste the image showing the simulated waveforms for FSM (Behavioral Simulation). Clearly show the LEFT turn and RIGHT turn Cases.


Answer:

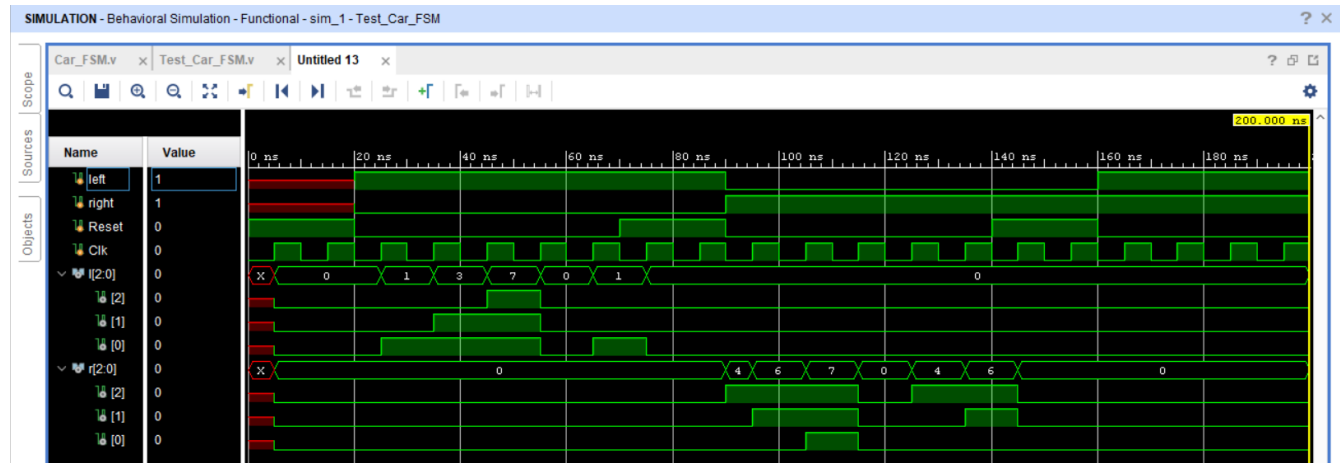

4. Add clock division code to **Car_FSM.v** such that the actual input **Clk (Y9 pin with frequency of 100MHz)** is converted to Clock of frequency 2Hz (or 4Hz). This 2Hz (or 4Hz) signal is used as clock for running the FSM. Connect the new (2Hz or 4Hz) clock as output of **Car_FSM.v** for reference.
5. Plan your I/O mapping (using **I/O planning** option) such that actual input **Clk** is connected to internal clock pin **Y9**, **Reset** is connected to push button switch, other inputs (**LEFT** and **RIGHT**) are connected to DIP switches and outputs are connected to LEDs. In the ZedBoard, the pin numbers indicating the DIP switches, LEDs and internal clock are listed in table uploaded in CMS. Save the mapping information as **Car_FSM.xdc**.
6. Synthesize (**Run Synthesis**).


Question: Paste the image showing the schematic after synthesis.

Answer:

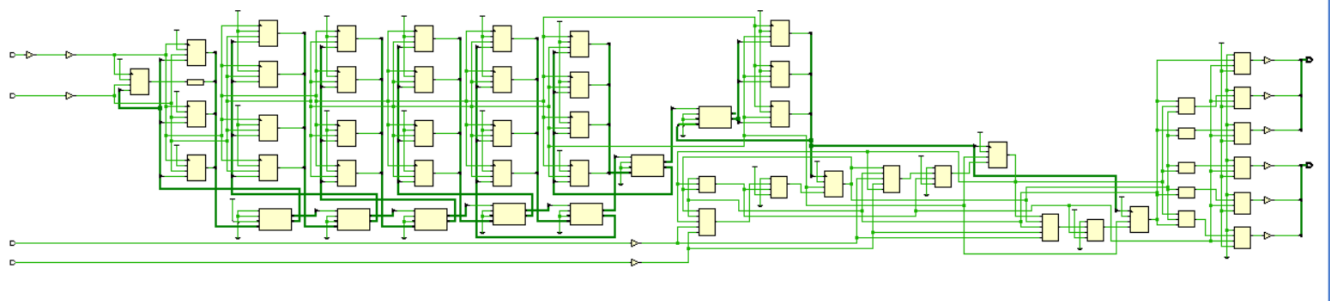


Question: Paste the image showing the Post-Synthesis Simulation for FSM.

Answer:

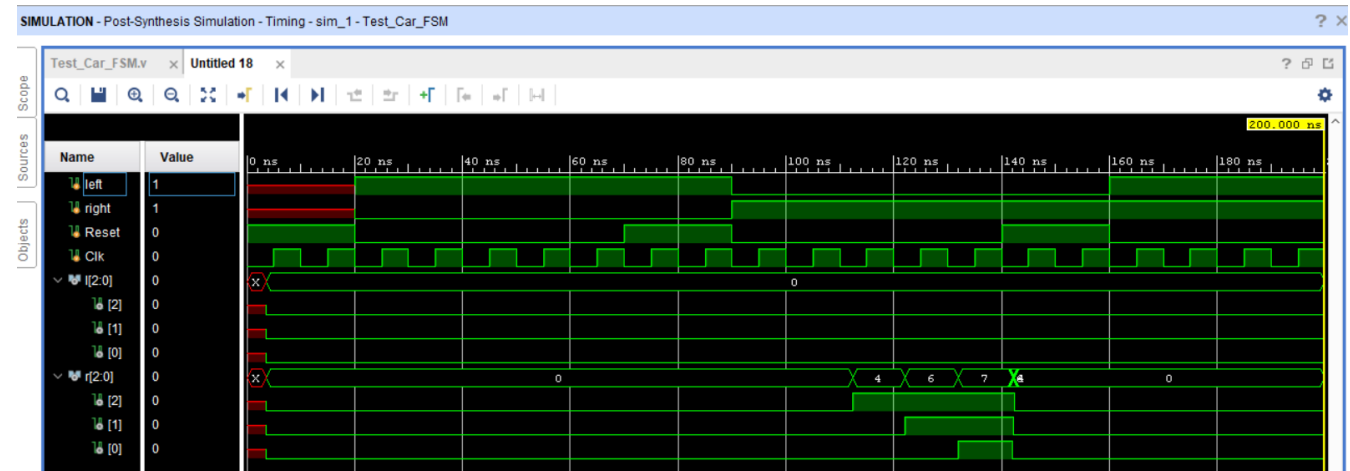

Question: Check the summary report and report hardware utilization for the FSM implementation.


Answer:

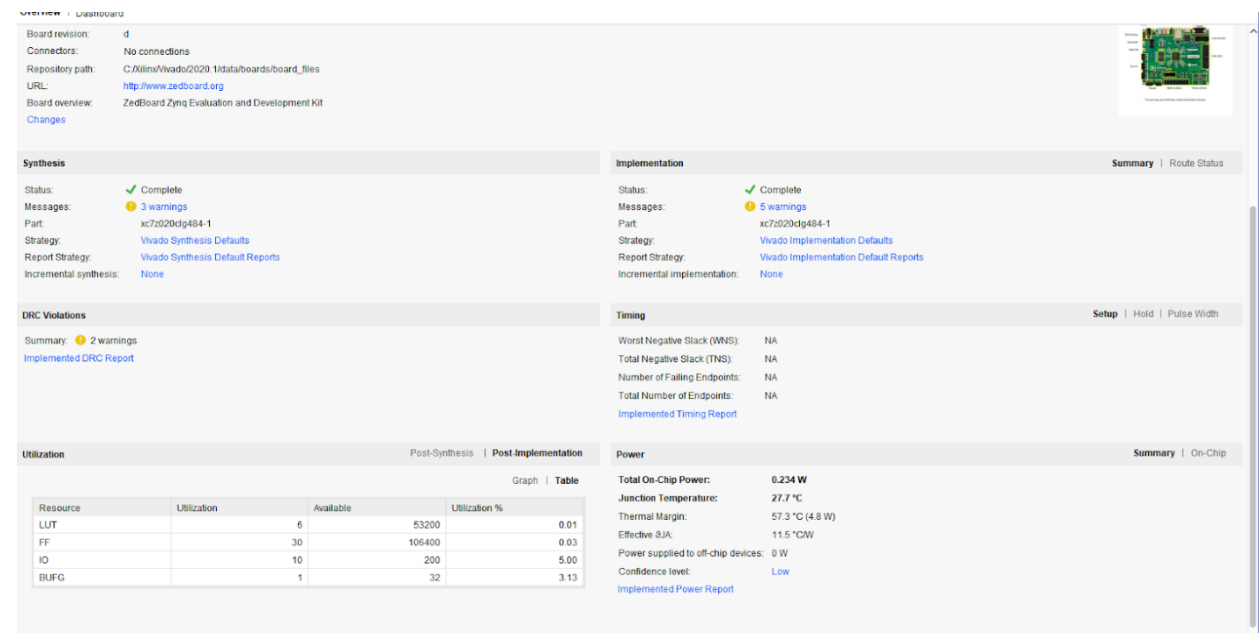

7. Implement the design (Run Implementation).


Question: Paste the image showing the Post-Implementation Simulation for FSM.

Answer:

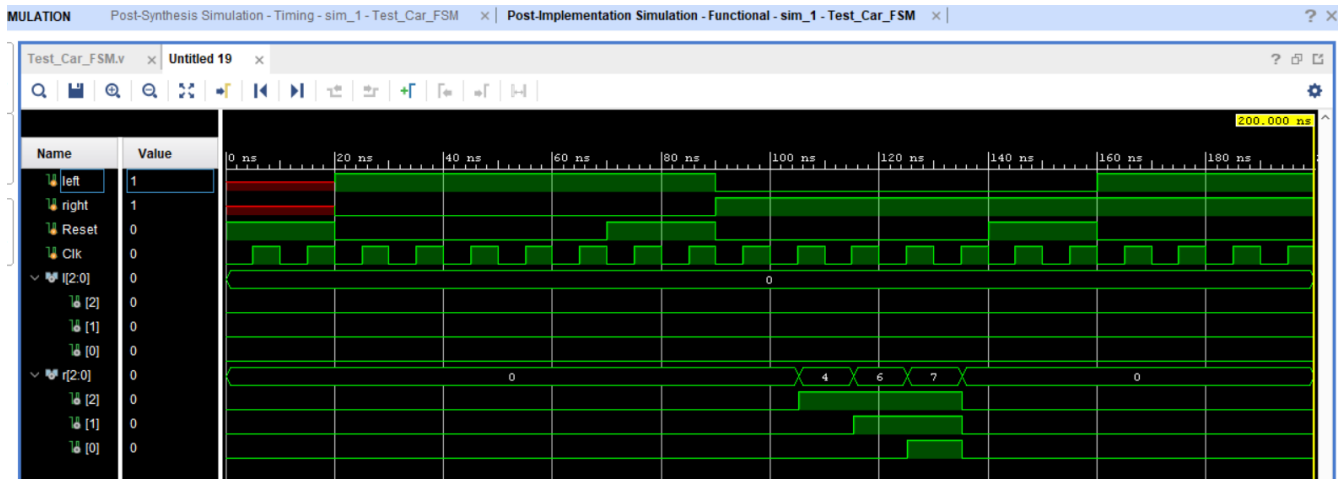

Question: Paste the image showing the Post-Implementation timing Simulation for FSM.

Answer:

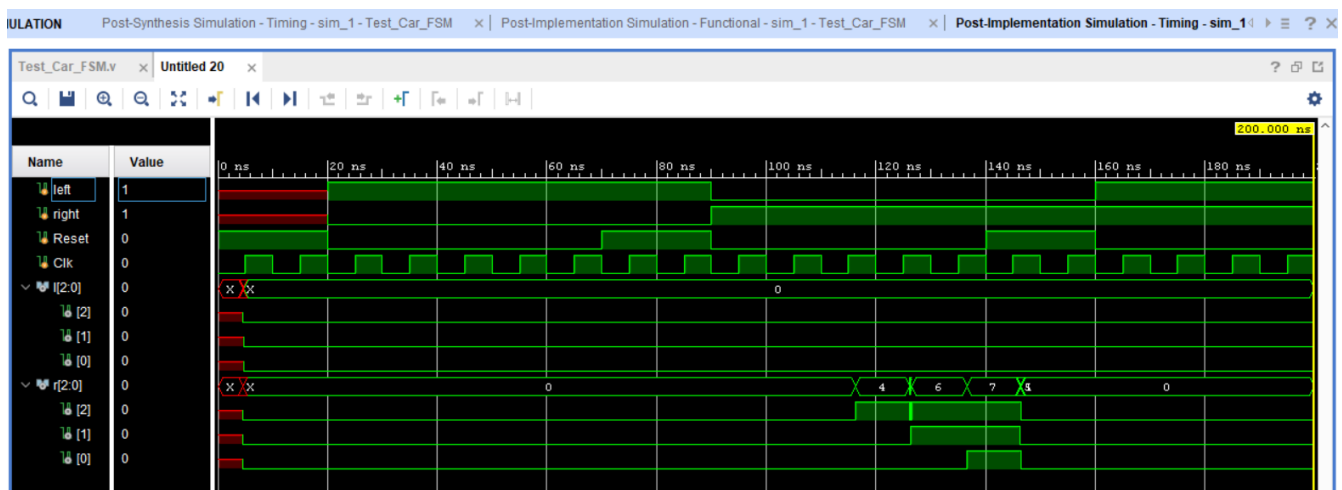

Question: Justify the difference between Post-Implementation and Post-Implementation timing Simulation waveforms.

Answer: Timing simulation is to verify whether the circuit will work at the required speed. Functional simulation is to verify the design of our circuit.

8. **Generate Bitstream** and port your design on to FPGA (**Open Hardware Manager** ☐ **New Target** ☐ ... **Program Device**)
9. **Check the output on FPGA.**

10. Show the output to the instructor.

11. Submit following files as a Zipped folder with file name as <Student1_ID_No>_<Student2_ID_No>.zip through CMS before due date.

- 1) Completed Document**
- 2) Car_FSM.v (with proper comments)**
- 3) Test_Car_FSM.v (with proper comments)**
- 4) Car_FSM.xdc.**